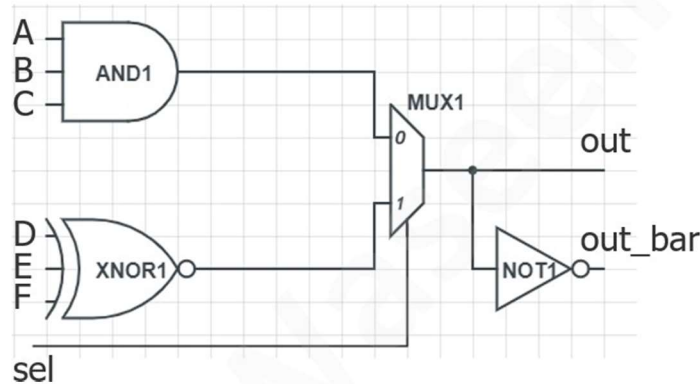


# Combinational Circuit Design

Design the following circuits with Verilog using assign statements.

1)

- The design has 7 inputs and 2 outputs
- Use assign statements to design the following



2) Implement 4-bit adder using addition operator

- The design takes 2 inputs (**A**, **B**) and the summation is assigned to output (**C**) ignoring the carry

3) Implement 2-to-4 Decoder using conditional operator (A logic decoder has  $n$  input lines and  $2^n$  output lines. Each output line corresponds to a unique combination of the input values.)

- The design has input **A** (2 bits) and output **D** (4 bits)

$A_1$	$A_0$	$D_3$	$D_2$	$D_1$	$D_0$
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

4) Implement an even parity generator module. In case you don't know what a parity bit is, please check this [link](#). The design input is a bus where a reduction operator will be used to generate the even parity bit.

- The design has 1 input **A** (8 bits) and 1 output **out\_with\_parity** (9 bit) where the parity bit calculated will be inserted in the least significant bit of the output bus and the remaining bits will be the input A (Hint: use concatenation).

5) Implement a comparator that compares 2 inputs (**A, B**) and has 3 outputs using conditional operator.

- The first output **A\_greaterthan\_B** is high only when A is greater than B
- The second output **A\_equals\_B** is high only when A equals B
- The third output **A\_lessthan\_B** is high only when A is less than B



Inputs A and B are 4-bit bus while the 3 outputs are single bits.

**Deliverables:** The assignment should be submitted as a PDF file with this format <your\_name>\_Assignment1.

Note that your document should be organized as 5 sections corresponding to each design above, and in each section, I am expecting the Verilog code for the design, and waveform snippets forcing different input values to verify the functionality of the design.