


	ASSINMENT 2	
--	-------------	--

	GROUP		NAME	
	1		Ahmed Khalaf Mohamed Ali	

1)

Ln#	
1	module MUX_ASS2(
2	input [2:0]D,
3	input A,B,C,sel,
4	output out,out_bar
5);
6	wire AND1,OR1,XNOR1;
7	and(AND1,D[0],D[1]);
8	or(OR1,AND1,D[2]);
9	xnor(XNOR1,A,B,C);
10	assign out=(sel)?XNOR1:OR1;
11	assign out_bar=~out;
12	endmodule
13	

Ln#	
1	module MUX_ASS2_tb();
2	/*wire and reg*/
3	reg [2:0]D;
4	reg A,B,C,sel;
5	wire out,out_bar;
6	/*instantiation*/
7	MUX_ASS2 DUT (D,A,B,C,sel,out,out_bar);
8	/*values*/
9	integer i;
10	initial begin
11	for(i=0 ; i<255; i=i+1) begin
12	D=\$random;
13	A=\$random;
14	B=\$random;
15	C=\$random;
16	sel=\$random;
17	#100;
18	end
19	\$stop;
20	end
21	initial begin
22	\$monitor("D=%b, A=%b, B=%b, C=%b, sel=%b, out=%b, out_bar=%b", D, A, B, C, sel, out, out_bar);
23	end
24	
25	endmodule
26	

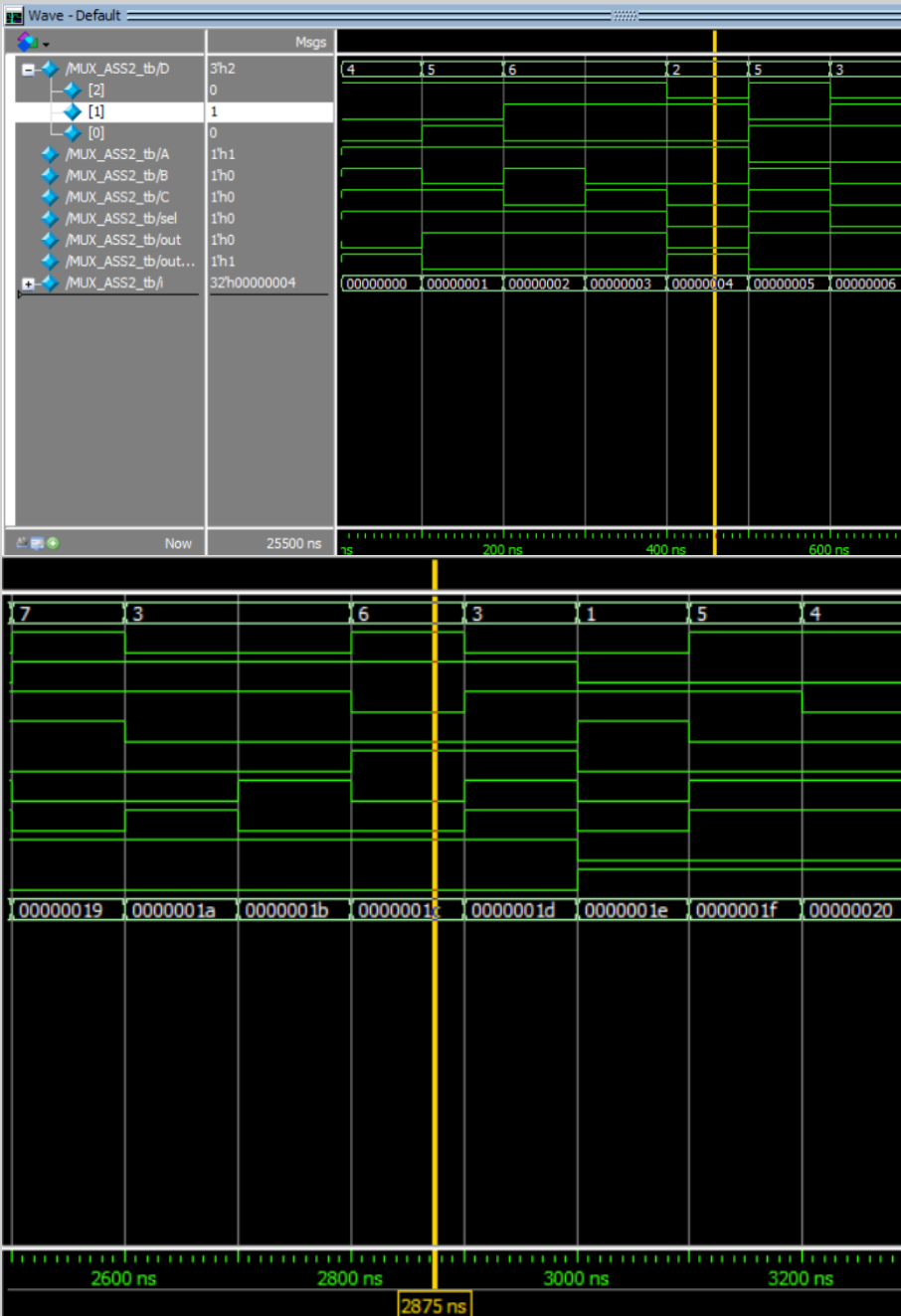

```

# D=011, A=1, B=0, C=0, sel=0, out=1, out_bar=0
# D=100, A=0, B=1, C=1, sel=1, out=1, out_bar=0
# D=110, A=0, B=0, C=1, sel=0, out=1, out_bar=0
# D=011, A=0, B=1, C=1, sel=1, out=1, out_bar=0
# D=001, A=0, B=1, C=1, sel=0, out=0, out_bar=1
# D=010, A=1, B=0, C=0, sel=0, out=0, out_bar=1
# D=101, A=0, B=0, C=1, sel=0, out=1, out_bar=0
# D=101, A=1, B=1, C=0, sel=1, out=1, out_bar=0
# D=100, A=1, B=1, C=1, sel=0, out=1, out_bar=0
# D=100, A=0, B=0, C=0, sel=0, out=1, out_bar=0
# D=010, A=1, B=1, C=1, sel=1, out=0, out_bar=1
# D=011, A=1, B=1, C=0, sel=0, out=1, out_bar=0
# D=111, A=1, B=1, C=0, sel=1, out=1, out_bar=0
# D=001, A=0, B=1, C=0, sel=1, out=0, out_bar=1
# D=101, A=1, B=0, C=1, sel=0, out=1, out_bar=0
# D=101, A=1, B=0, C=0, sel=0, out=1, out_bar=0
# D=111, A=0, B=0, C=0, sel=0, out=1, out_bar=0
# D=000, A=1, B=0, C=0, sel=0, out=0, out_bar=1
# D=111, A=0, B=1, C=1, sel=0, out=1, out_bar=0
# D=101, A=0, B=0, C=0, sel=0, out=1, out_bar=0
# D=101, A=1, B=1, C=1, sel=0, out=1, out_bar=0
# D=110, A=1, B=0, C=1, sel=1, out=1, out_bar=0
# D=111, A=0, B=1, C=1, sel=0, out=1, out_bar=0
# D=001, A=1, B=1, C=1, sel=0, out=0, out_bar=1
# D=110, A=0, B=1, C=1, sel=1, out=1, out_bar=0
# D=100, A=1, B=0, C=0, sel=1, out=0, out_bar=1
# D=001, A=0, B=0, C=1, sel=0, out=0, out_bar=1
# D=011, A=0, B=1, C=1, sel=0, out=1, out_bar=0
# D=001, A=1, B=1, C=0, sel=0, out=0, out_bar=1
# D=010, A=1, B=0, C=0, sel=1, out=0, out_bar=1
# D=000, A=0, B=1, C=0, sel=0, out=0, out_bar=1
# ** Note: $stop      : C:/questasim64_2021.1/examples/MUX_ASS2_tb.v(19)
#   Time: 25500 ns   Iteration: 0   Instance: /MUX_ASS2_tb
# Break in Module MUX_ASS2_tb at C:/questasim64_2021.1/examples/MUX_ASS2_tb.v line 19

```

2)


```

C:/questasim64_2021.1/examples/priority_encoder.v (/PRIORITY_ENCODER_tb/DUT) - Default :
Ln#
1  module PRIORITY_ENCODER(X,Y) ;
2      input  [3:0] X;
3      output reg [1:0] Y;
4      always @(X) begin
5          casex(X)
6              4'b1xxx : Y=2'b11;
7              4'b01xx : Y=2'b10;
8              4'b001x : Y=2'b01;
9              4'b000x : Y=2'b00;
10         endcase
11     end
12 endmodule
13

```

```
C:/questasim64_2021.1/examples/priority_encoder_tb.v (/PRIORITY_ENCODER_tb) - Default
Ln#
3   reg [1:0] Y_EXPECTED;
4   wire [1:0] Y_tb;
5   PRIORITY_ENCODER DUT(X_tb,Y_tb);
6   /*initial */
7   integer i;
8   initial begin
9   for(i=0 ; i<99; i=i+1) begin
10    X_tb=$random;
11    #10;
12    casex(X_tb)
13    4'b1xxx : Y_EXPECTED=2'b11;
14    4'b01xx : Y_EXPECTED=2'b10;
15    4'b001x : Y_EXPECTED=2'b01;
16    4'b000x : Y_EXPECTED=2'b00;
17    endcase
18    if(Y_EXPECTED != Y_tb) begin
19    $display("error ,there are some thing not correctl");
20    end
21
22    end
23    $stop;
24    end
25    initial begin
26
27        $monitor("X_tb=%b,Y_EXPECTED=%b,Y_tb=%b",X_tb,Y_EXPECTED,Y_tb);
28
29    end
30    endmodule
31
```

```
C:/questasim64_2021.1/examples/priority_encoder_tb.v (/PRIORITY_ENCODER_tb) - Default
Ln#
4   wire [1:0] Y_tb;
5   PRIORITY_ENCODER DUT(X_tb,Y_tb);
6   /*initial */
7   integer i;
8   initial begin
9   for(i=0 ; i<99; i=i+1) begin
10    X_tb=$random;
11    #0;
12    casex(X_tb)
13    4'b1xxx : Y_EXPECTED=2'b11;
14    4'b01xx : Y_EXPECTED=2'b10;
15    4'b001x : Y_EXPECTED=2'b01;
16    4'b000x : Y_EXPECTED=2'b00;
17    endcase
18    if(Y_EXPECTED != Y_tb) begin
19    $display("error ,there are some thing not correctl");
20    end
21    #10;
22    end
23    X_tb=4'b1111; Y_EXPECTED=2'b00;
24    if(Y_EXPECTED != Y_tb) begin
25    $display("error ,there are some thing not correctl");
26    end
27    $stop;
28    end
29    initial begin
30
31        $monitor("X_tb=%b,Y_EXPECTED=%b,Y_tb=%b",X_tb,Y_EXPECTED,Y_tb);
32
33    end
34    endmodule
35
```

 

```

# X_tb=1010,Y_EXPECTED=11,Y_tb=11
# X_tb=1110,Y_EXPECTED=11,Y_tb=11
# X_tb=0101,Y_EXPECTED=10,Y_tb=10
# X_tb=0001,Y_EXPECTED=00,Y_tb=00
# X_tb=1001,Y_EXPECTED=11,Y_tb=11
# X_tb=0010,Y_EXPECTED=01,Y_tb=01
# X_tb=1100,Y_EXPECTED=11,Y_tb=11
# X_tb=1111,Y_EXPECTED=11,Y_tb=11
# X_tb=1000,Y_EXPECTED=11,Y_tb=11
# X_tb=0111,Y_EXPECTED=10,Y_tb=10
# X_tb=1111,Y_EXPECTED=11,Y_tb=11
# X_tb=1100,Y_EXPECTED=11,Y_tb=11
# X_tb=1011,Y_EXPECTED=11,Y_tb=11
# X_tb=1001,Y_EXPECTED=11,Y_tb=11
# X_tb=0000,Y_EXPECTED=00,Y_tb=00
# X_tb=0111,Y_EXPECTED=10,Y_tb=10
# X_tb=0001,Y_EXPECTED=00,Y_tb=00
# X_tb=0110,Y_EXPECTED=10,Y_tb=10
# X_tb=1100,Y_EXPECTED=11,Y_tb=11
# X_tb=0010,Y_EXPECTED=01,Y_tb=01
# X_tb=1000,Y_EXPECTED=11,Y_tb=11
# X_tb=0111,Y_EXPECTED=10,Y_tb=10
# X_tb=1101,Y_EXPECTED=11,Y_tb=11
# X_tb=0010,Y_EXPECTED=01,Y_tb=01
# X_tb=1110,Y_EXPECTED=11,Y_tb=11
# X_tb=1101,Y_EXPECTED=11,Y_tb=11
# X_tb=1001,Y_EXPECTED=11,Y_tb=11
# X_tb=1111,Y_EXPECTED=11,Y_tb=11
# X_tb=0011,Y_EXPECTED=01,Y_tb=01
# X_tb=0101,Y_EXPECTED=10,Y_tb=10
# error .there are some thing not correctl

```

3)

```

C:/questasim64_2021.1/examples/BCD.v (/BCD_tb/DUT1) - Default
Ln#
1  module BCD(D0,D1,D2,D3,D4,D5,D6,D7,D8,D9,Y0,Y1,Y2,Y3);
2  input  D0,D1,D2,D3,D4,D5,D6,D7,D8,D9;
3  output reg Y0,Y1,Y2,Y3;
4  always @(*) begin
5  case ({D9,D8,D7,D6,D5,D4,D3,D2,D1,D0})
6  1: {Y3,Y2,Y1,Y0}=0;
7  2: {Y3,Y2,Y1,Y0}=1;
8  4: {Y3,Y2,Y1,Y0}=2;
9  8: {Y3,Y2,Y1,Y0}=3;
10 16: {Y3,Y2,Y1,Y0}=4;
11 32: {Y3,Y2,Y1,Y0}=5;
12 64: {Y3,Y2,Y1,Y0}=6;
13 128: {Y3,Y2,Y1,Y0}=7;
14 256: {Y3,Y2,Y1,Y0}=8;
15 512: {Y3,Y2,Y1,Y0}=9;
16 default : {Y3,Y2,Y1,Y0}=0;
17 endcase
18 end
19 endmodule
20

```


C:/questasim64_2021.1/examples/BCD2.v (/BCD_tb/DUT2) - Default

```


Ln#
1 module BCD2(D0,D1,D2,D3,D4,D5,D6,D7,D8,D9,Y0,Y1,Y2,Y3);
2   input D0,D1,D2,D3,D4,D5,D6,D7,D8,D9;
3   output reg Y0,Y1,Y2,Y3;
4
5   always @(*) begin
6       if ({D9,D8,D7,D6,D5,D4,D3,D2,D1,D0} == 10'b0000000001)
7           {Y3,Y2,Y1,Y0} = 4'b0000;
8       else if ({D9,D8,D7,D6,D5,D4,D3,D2,D1,D0} == 10'b0000000010)
9           {Y3,Y2,Y1,Y0} = 4'b0001;
10      else if ({D9,D8,D7,D6,D5,D4,D3,D2,D1,D0} == 10'b0000000100)
11          {Y3,Y2,Y1,Y0} = 4'b0010;
12      else if ({D9,D8,D7,D6,D5,D4,D3,D2,D1,D0} == 10'b00000001000)
13          {Y3,Y2,Y1,Y0} = 4'b0011;
14      else if ({D9,D8,D7,D6,D5,D4,D3,D2,D1,D0} == 10'b00000010000)
15          {Y3,Y2,Y1,Y0} = 4'b0100;
16      else if ({D9,D8,D7,D6,D5,D4,D3,D2,D1,D0} == 10'b00000100000)
17          {Y3,Y2,Y1,Y0} = 4'b0101;
18      else if ({D9,D8,D7,D6,D5,D4,D3,D2,D1,D0} == 10'b00010000000)
19          {Y3,Y2,Y1,Y0} = 4'b0110;
20      else if ({D9,D8,D7,D6,D5,D4,D3,D2,D1,D0} == 10'b00100000000)
21          {Y3,Y2,Y1,Y0} = 4'b0111;
22      else if ({D9,D8,D7,D6,D5,D4,D3,D2,D1,D0} == 10'b01000000000)
23          {Y3,Y2,Y1,Y0} = 4'b1000;
24      else if ({D9,D8,D7,D6,D5,D4,D3,D2,D1,D0} == 10'b10000000000)
25          {Y3,Y2,Y1,Y0} = 4'b1001;
26      else
27          {Y3,Y2,Y1,Y0} = 4'b0000;
28   end
29
30 endmodule
31


```

```

Ln#
1 module BCD_tb();
2   reg D0,D1,D2,D3,D4,D5,D6,D7,D8,D9;
3   wire Y0,Y1,Y2,Y3;
4   wire Y0_t0,Y1_t0,Y2_t0,Y3_t0;
5   BCD DUT1(D0,D1,D2,D3,D4,D5,D6,D7,D8,D9,Y0_t0,Y1_t0,Y2_t0,Y3_t0);
6   BCD DUT2(D0,D1,D2,D3,D4,D5,D6,D7,D8,D9,Y0_t0,Y1_t0,Y2_t0,Y3_t0);
7   integer i;
8   initial begin
9       #0 (D0,D1,D2,D3,D4,D5,D6,D7,D8,D9)=2;
10      if(({Y0_t0,Y1_t0,Y2_t0,Y3_t0} != {Y0_t0,Y1_t0,Y2_t0,Y3_t0})) begin
11          $display("error ,there are some thing not correct!");
12      end
13      #10;
14      for(i=0 ; i<255; i=i+1) begin
15          {D0,D1,D2,D3,D4,D5,D6,D7,D8,D9}=i;
16          if(({Y0_t0,Y1_t0,Y2_t0,Y3_t0} != {Y0_t0,Y1_t0,Y2_t0,Y3_t0})) begin
17              $display("error ,there are some thing not correct!");
18          end
19          #10;
20      end
21      $stop;
22   end
23   initial begin
24       $monitor("D0_t0,D1_t0,D2_t0,D3_t0,D4_t0,D5_t0,D6_t0,D7_t0,D8_t0,D9_t0={b},{Y0_t0,Y1_t0,Y2_t0,Y3_t0}={b},{Y0_t0,Y1_t0,Y2_t0,Y3_t0}={b}",
25               {D0_t0,D1_t0,D2_t0,D3_t0,D4_t0,D5_t0,D6_t0,D7_t0,D8_t0,D9_t0},{Y0_t0,Y1_t0,Y2_t0,Y3_t0},{Y0_t0,Y1_t0,Y2_t0,Y3_t0});
26   end
27 endmodule
28

```

 


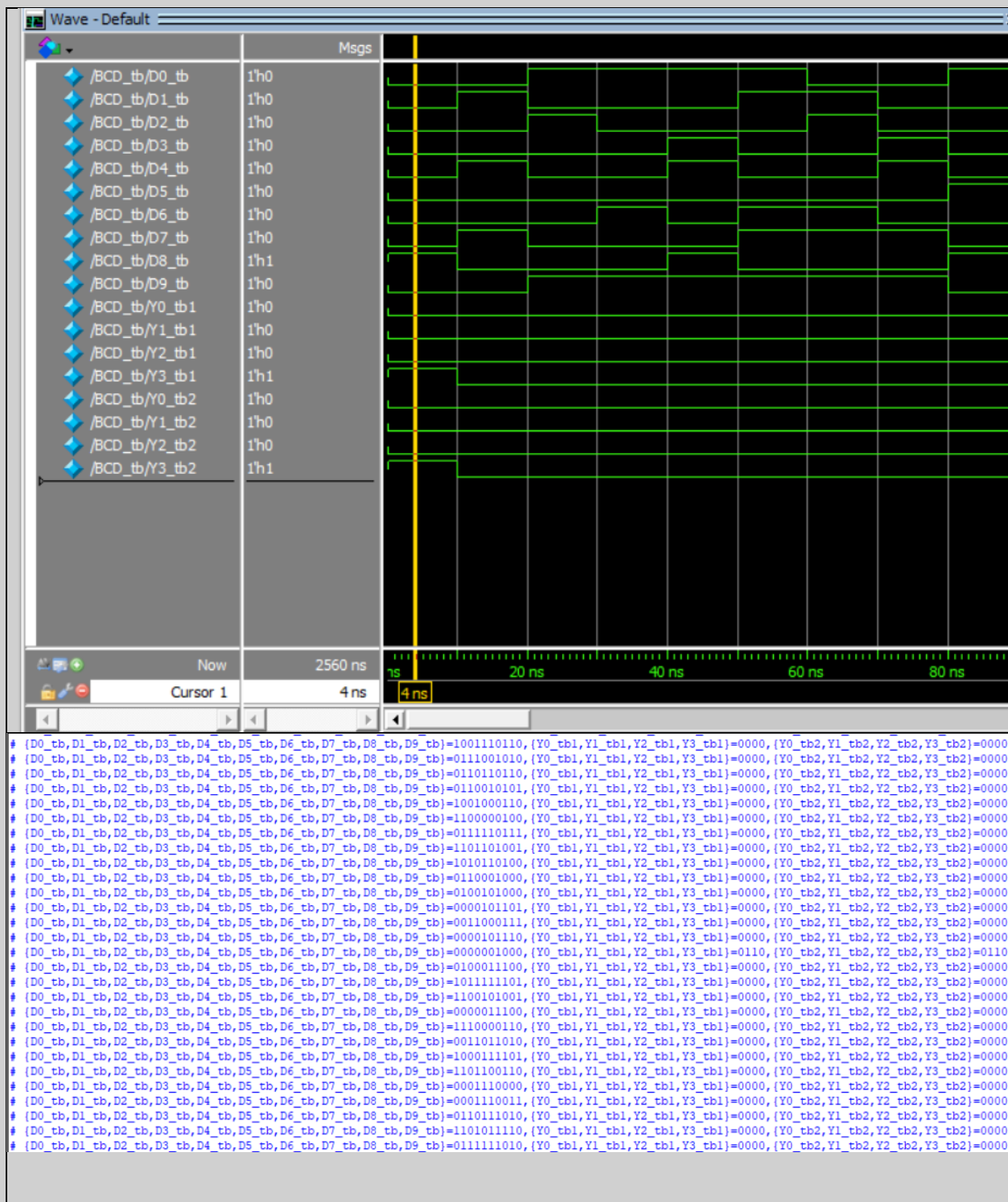

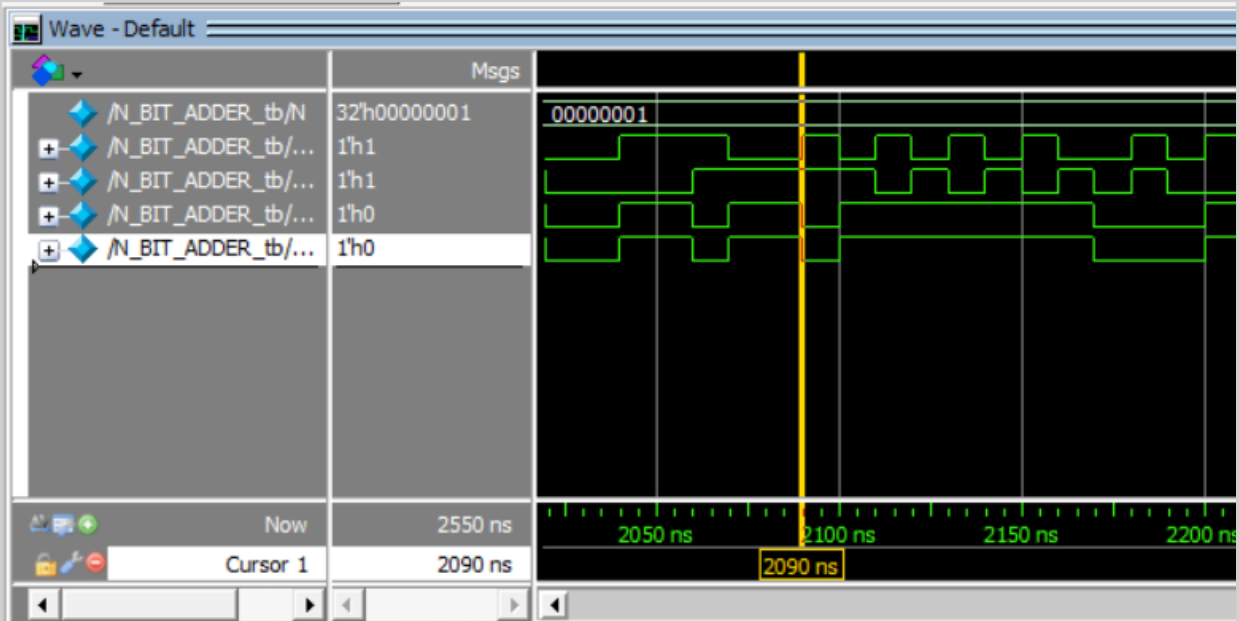4)

```
C:/questasim64_2021.1/examples/N_BIT_ADDER.v (/N_BIT_ADDER_tb/DUT)
Ln#
1 module N_BIT_ADDER (A,B,C);
2   parameter N=1;
3   input [N-1:0] A;
4   input [N-1:0] B;
5   input [N-1:0] C;
6   assign C=A+B;
7   endmodule
8
```

```
C:/questasim64_2021.1/examples/N_BIT_ADDER_tb.v (/N_BIT_ADDER_tb) - Default *
Ln#
1 module N_BIT_ADDER_tb();
2   parameter N=1;
3   reg [N-1:0] A_tb;
4   reg [N-1:0] B_tb;
5   reg [N-1:0] Y_expected;
6   wire [N-1:0] C_tb;
7   N_BIT_ADDER #(.N(N)) DUT (A_tb,B_tb,C_tb);
8   integer i;
9   initial begin
10
11   for(i=0 ; i<4; i=i+1) begin
12     A_tb=$random;
13     B_tb=$random;
14     Y_expected=A_tb+B_tb;
15   if( C_tb != Y_expected) begin
16     $display("error ,there are some thing not correct!");
17   end
18   #10;
19   end
20   $stop;
21   end
22   initial begin
23     $monitor ("A_tb=%b,B_tb=%b,Y_expected=%b,C_tb=%b",A_tb,B_tb,Y_expected,C_tb);
24   end
25   endmodule
26
```



Transcript

```
# A_tb=1,B_tb=0,Y_expected=1,C_tb=1
# A_tb=0,B_tb=1,Y_expected=1,C_tb=1
# A_tb=1,B_tb=0,Y_expected=1,C_tb=1
# A_tb=1,B_tb=1,Y_expected=0,C_tb=0
# A_tb=0,B_tb=1,Y_expected=1,C_tb=1
# A_tb=1,B_tb=1,Y_expected=0,C_tb=0
# A_tb=0,B_tb=1,Y_expected=1,C_tb=1
# A_tb=1,B_tb=1,Y_expected=0,C_tb=0
# A_tb=0,B_tb=0,Y_expected=0,C_tb=0
# A_tb=1,B_tb=0,Y_expected=1,C_tb=1
# A_tb=0,B_tb=1,Y_expected=1,C_tb=1
# A_tb=0,B_tb=0,Y_expected=0,C_tb=0
# A_tb=1,B_tb=1,Y_expected=0,C_tb=0
# A_tb=0,B_tb=1,Y_expected=1,C_tb=1
# A_tb=1,B_tb=1,Y_expected=0,C_tb=0
# A_tb=1,B_tb=0,Y_expected=1,C_tb=1
# A_tb=0,B_tb=1,Y_expected=1,C_tb=1
# A_tb=1,B_tb=1,Y_expected=0,C_tb=0
# A_tb=0,B_tb=0,Y_expected=0,C_tb=0
# A_tb=1,B_tb=0,Y_expected=1,C_tb=1
# A_tb=0,B_tb=1,Y_expected=1,C_tb=1
# A_tb=1,B_tb=1,Y_expected=0,C_tb=0
# A_tb=0,B_tb=0,Y_expected=0,C_tb=0
# A_tb=1,B_tb=0,Y_expected=1,C_tb=1
# A_tb=0,B_tb=1,Y_expected=1,C_tb=1
# A_tb=1,B_tb=1,Y_expected=0,C_tb=0
# A_tb=0,B_tb=0,Y_expected=0,C_tb=0
# A_tb=1,B_tb=0,Y_expected=1,C_tb=1
# A_tb=0,B_tb=0,Y_expected=0,C_tb=0
# A_tb=1,B_tb=1,Y_expected=0,C_tb=0
# A_tb=1,B_tb=0,Y_expected=1,C_tb=1
# A_tb=0,B_tb=0,Y_expected=0,C_tb=0
# A_tb=1,B_tb=1,Y_expected=0,C_tb=0
# ** Note: $stop      : C:/questasim64_2021.1/examples/N_BIT_ADDER_tb.v(18)
#   Time: 2550 ns   Iteration: 0   Instance: /N_BIT_ADDER_tb
# Break in Module N_BIT_ADDER_tb at C:/questasim64_2021.1/examples/N_BIT_ADDER_tb.v line 18
```

5)

```
C:/questasim64_2021.1/examples/N_bit_ALU.v (/N_BIT_ALU_tb/DUT) - Default
Ln#
1  module N_BIT_ALU(A,B,opcode,result);
2      parameter N_ALU=4;
3      input [N_ALU-1:0] A;
4      input [N_ALU-1:0] B;
5      input [1:0] opcode;
6      output reg [N_ALU-1:0] result;
7      wire [N_ALU-1:0] ADD_signal;
8      N_BIT_ADDER #(N(N_ALU)) ADDERO(.A(A),.B(B),.C(ADD_signal));
9      always @(*) begin
10         case (opcode)
11             2'b00: result = ADD_signal;
12             2'b01: result = A | B;
13             2'b10: result = A-B;
14             2'b11: result = A^B;
15         endcase
16     end
17 endmodule
18
```



```

# A_tb=1000,B_tb=1011,opcode_tb=11,Y_expected=0011,result_tb=0011
# A_tb=1100,B_tb=1010,opcode_tb=10,Y_expected=0010,result_tb=0010
# A_tb=1000,B_tb=1001,opcode_tb=01,Y_expected=1001,result_tb=1001
# A_tb=1110,B_tb=0110,opcode_tb=11,Y_expected=1000,result_tb=1000
# A_tb=1010,B_tb=1010,opcode_tb=01,Y_expected=1010,result_tb=1010
# A_tb=1110,B_tb=1000,opcode_tb=01,Y_expected=1110,result_tb=1110
# A_tb=1000,B_tb=1010,opcode_tb=11,Y_expected=0010,result_tb=0010
# A_tb=1011,B_tb=0111,opcode_tb=10,Y_expected=0100,result_tb=0100
# A_tb=1010,B_tb=0100,opcode_tb=01,Y_expected=1110,result_tb=1110
# A_tb=0010,B_tb=0100,opcode_tb=11,Y_expected=0110,result_tb=0110
# A_tb=0110,B_tb=1010,opcode_tb=10,Y_expected=1100,result_tb=1100
# A_tb=0010,B_tb=1101,opcode_tb=00,Y_expected=1111,result_tb=1111
# A_tb=0100,B_tb=1010,opcode_tb=01,Y_expected=1110,result_tb=1110
# A_tb=0001,B_tb=1110,opcode_tb=11,Y_expected=1111,result_tb=1111
# A_tb=1011,B_tb=1111,opcode_tb=01,Y_expected=1111,result_tb=1111
# A_tb=0110,B_tb=0101,opcode_tb=11,Y_expected=0011,result_tb=0011
# A_tb=1011,B_tb=1000,opcode_tb=10,Y_expected=0011,result_tb=0011
# A_tb=1011,B_tb=0010,opcode_tb=00,Y_expected=1101,result_tb=1101
# A_tb=1101,B_tb=1011,opcode_tb=10,Y_expected=0010,result_tb=0010
# A_tb=1110,B_tb=1101,opcode_tb=00,Y_expected=1011,result_tb=1011
# A_tb=1000,B_tb=0001,opcode_tb=10,Y_expected=0111,result_tb=0111
# A_tb=0001,B_tb=1011,opcode_tb=00,Y_expected=1100,result_tb=1100
# A_tb=0011,B_tb=0110,opcode_tb=11,Y_expected=0101,result_tb=0101
# A_tb=0010,B_tb=0100,opcode_tb=11,Y_expected=0110,result_tb=0110
# A_tb=1000,B_tb=0010,opcode_tb=00,Y_expected=1010,result_tb=1010
# A_tb=1001,B_tb=0101,opcode_tb=01,Y_expected=1101,result_tb=1101
# A_tb=1011,B_tb=0001,opcode_tb=00,Y_expected=1100,result_tb=1100
# A_tb=0111,B_tb=0001,opcode_tb=11,Y_expected=0110,result_tb=0110
# A_tb=0100,B_tb=1000,opcode_tb=10,Y_expected=1100,result_tb=1100
# A_tb=0100,B_tb=0010,opcode_tb=10,Y_expected=0010,result_tb=0010
# ** Note: $stop      : C:/questasim64_2021.1/examples/N_BIT_ALU_tb.v(29)
#   Time: 1485 ns   Iteration: 0   Instance: /N_BIT_ALU_tb
# Break in Module N_BIT_ALU_tb at C:/questasim64_2021.1/examples/N_BIT_ALU_tb.v line 29

```


6)

```

Ln#
1  module SEVEN_SEGMENT(A,B,opcode,enable,a,b,c,d,e,f,g);
2      parameter N_ALU=4;
3      input  [N_ALU-1:0] A;
4      input  [N_ALU-1:0] B;
5      input  [1:0] opcode;
6      input  enable;
7      output reg a,b,c,d,e,f,g;
8      wire  [N_ALU-1:0] ADD_signal;
9      N_BIT_ALU #(N_ALU(N_ALU)) ALU1(.A(A),.B(B),.opcode(opcode),.result(ADD_signal));
10     always @(*) begin
11         if(enable)
12             case(ADD_signal)
13                 0: {a,b,c,d,e,f,g}=7'b1111110;
14                 1: {a,b,c,d,e,f,g}=7'b0110000;
15                 2: {a,b,c,d,e,f,g}=7'b1101101;
16                 3: {a,b,c,d,e,f,g}=7'b1111001;//
17                 4: {a,b,c,d,e,f,g}=7'b0110011;//
18                 5: {a,b,c,d,e,f,g}=7'b1011011;//
19                 6: {a,b,c,d,e,f,g}=7'b1011111;//
20                 7: {a,b,c,d,e,f,g}=7'b1110000;//
21                 8: {a,b,c,d,e,f,g}=7'b1111111;//
22                 9: {a,b,c,d,e,f,g}=7'b1111011;//
23                 4'hA: {a,b,c,d,e,f,g}=7'b1110111;
24                 4'hB: {a,b,c,d,e,f,g}=7'b0011111;
25                 4'hC: {a,b,c,d,e,f,g}=7'b1001110;//
26                 4'hD: {a,b,c,d,e,f,g}=7'b0111101;//
27                 4'hE: {a,b,c,d,e,f,g}=7'b1001111;
28                 4'hF: {a,b,c,d,e,f,g}=7'b1000111;
29                 default : {a,b,c,d,e,f,g}=7'b0000000;
30             endcase
31         else
32             {a,b,c,d,e,f,g}=7'b0000000;
33         end
34     endmodule
35

```

```

1  module SEVEN_SEGMENT_tb();
2      parameter N_ALU_tb=4;
3      reg [N_ALU_tb-1:0] A_tb;
4      reg [N_ALU_tb-1:0] B_tb;
5      reg enable_tb;
6      reg [1:0] opcode_tb;
7      reg [6:0] Y_expected;
8      wire a_tb,b_tb,c_tb,d_tb,e_tb,f_tb,g_tb;
9      //wire [N_ALU_tb-1:0] result_tb;
10     SEVEN_SEGMENT #(N_ALU_tb) DUT (.A(A_tb),
11         .B(B_tb),
12         .opcode(opcode_tb),
13         .enable(enable_tb),
14         .a(a_tb),
15         .b(b_tb),
16         .c(c_tb),
17         .d(d_tb),
18         .e(e_tb),
19         .f(f_tb),
20         .g(g_tb));
21     initial begin
22         #0 A_tb=0;B_tb=0;enable_tb=1;opcode_tb=0;Y_expected=7'b1111110;
23         #5;
24     if( {a_tb,b_tb,c_tb,d_tb,e_tb,f_tb,g_tb} != Y_expected) begin
25         $display("error ,there are some thing not correct!");
26         $stop;
27     end

```

```

28     #10;
29     A_tb=3;B_tb=2;enable_tb=1;opcode_tb=2;Y_expected=7'b0110000;
30     #5;
31     if( {a_tb,b_tb,c_tb,d_tb,e_tb,f_tb,g_tb} != Y_expected) begin
32         $display("error ,there are some thing not correct1");
33         $stop;
34     end
35     #10;
36     A_tb=2;B_tb=2;enable_tb=1;opcode_tb=1;Y_expected=7'b1101101;
37     #5;
38     if( {a_tb,b_tb,c_tb,d_tb,e_tb,f_tb,g_tb} != Y_expected) begin
39         $display("error ,there are some thing not correct1");
40         $stop;
41     end
42     #10;
43     A_tb=2;B_tb=1;opcode_tb=0;Y_expected=7'b1111001;
44     #5;
45     if( {a_tb,b_tb,c_tb,d_tb,e_tb,f_tb,g_tb} != Y_expected) begin
46         $display("error ,there are some thing not correct1");
47         $stop;
48     end
49     #10;
50     A_tb=0;B_tb=4;opcode_tb=11;Y_expected=7'b0110011;
51     #5;
52     if( {a_tb,b_tb,c_tb,d_tb,e_tb,f_tb,g_tb} != Y_expected) begin
53         $display("error ,there are some thing not correct1");
54         $stop;
55     end
56     #10;
57     A_tb=1;B_tb=4;opcode_tb=00;Y_expected=7'b1011011;
58     #5;
59     if( {a_tb,b_tb,c_tb,d_tb,e_tb,f_tb,g_tb} != Y_expected) begin
60         $display("error ,there are some thing not correct1");
61         $stop;
62     end
63     #10;
64     A_tb=2;B_tb=4;Y_expected=7'b1011111;
65     #5;
66     if( {a_tb,b_tb,c_tb,d_tb,e_tb,f_tb,g_tb} != Y_expected) begin
67         $display("error ,there are some thing not correct1");
68         $stop;
69     end

```

```



70     #10;
71     A_tb=6;B_tb=1;Y_expected=7'b1110000;
72     #5;
73     if( {a_tb,b_tb,c_tb,d_tb,e_tb,f_tb,g_tb} != Y_expected) begin
74         $display("error ,there are some thing not correct1");
75         $stop;
76     end
77     #10;
78     A_tb=6;B_tb=2;Y_expected=7'b1111111;
79     #5;
80     if( {a_tb,b_tb,c_tb,d_tb,e_tb,f_tb,g_tb} != Y_expected) begin
81         $display("error ,there are some thing not correct1");
82         $stop;
83     end
84     #10;
85     A_tb=6;B_tb=3;Y_expected=7'b1111011;
86     #5;
87     if( {a_tb,b_tb,c_tb,d_tb,e_tb,f_tb,g_tb} != Y_expected) begin
88         $display("error ,there are some thing not correct1");
89         $stop;
90     end
91     #10;
92     A_tb=4'hA;B_tb=0;Y_expected=7'b1110111;
93     #5;
94     if( {a_tb,b_tb,c_tb,d_tb,e_tb,f_tb,g_tb} != Y_expected) begin
95         $display("error ,there are some thing not correct1");
96         $stop;
97     end
98     #10;
99     A_tb=4'hA;B_tb=1;Y_expected=7'b0011111;
100    #5;
101    if( {a_tb,b_tb,c_tb,d_tb,e_tb,f_tb,g_tb} != Y_expected) begin
102        $display("error ,there are some thing not correct1");
103        $stop;
104    end
105    #10;
106    A_tb=4'hA;B_tb=2;Y_expected=7'b1001110;
107    #5;
108    if( {a_tb,b_tb,c_tb,d_tb,e_tb,f_tb,g_tb} != Y_expected) begin
109        $display("error ,there are some thing not correct1");
110        $stop;
111    end

```

```

112     #10;
113     A_tb=4'hA;B_tb=3;Y_expected=7'b0111101;
114     #5;
115     if( {a_tb,b_tb,c_tb,d_tb,e_tb,f_tb,g_tb} != Y_expected) begin
116         $display("error ,there are some thing not correct!");
117         $stop;
118     end
119     #10;
120     A_tb=4'hC;B_tb=2;Y_expected=7'b1001111;
121     #5;
122     if( {a_tb,b_tb,c_tb,d_tb,e_tb,f_tb,g_tb} != Y_expected) begin
123         $display("error ,there are some thing not correct!");
124         $stop;
125     end
126     #10;
127     A_tb=4'hB;B_tb=4;Y_expected=7'b1000111;
128     #5;
129     if( {a_tb,b_tb,c_tb,d_tb,e_tb,f_tb,g_tb} != Y_expected) begin
130         $display("error ,there are some thing not correct!");
131         $stop;
132     end
133     #10;
134     enable_tb=0;Y_expected=7'b0000000;
135     #5;
136     if( {a_tb,b_tb,c_tb,d_tb,e_tb,f_tb,g_tb} != Y_expected) begin
137         $display("error ,there are some thing not correct!");
138         $stop;
139     end
140     #10;
141     $stop;
142 end
143 initial begin
144     $monitor ("A_tb=%b, B_tb=%b, opcode_tb=%b, enable_tb=%b, Y_expected=%b, {a_tb, b_tb, c_tb, d_tb, e_tb, f_tb, g_tb}=%b",
145     A_tb, B_tb, opcode_tb, enable_tb, Y_expected, {a_tb, b_tb, c_tb, d_tb, e_tb, f_tb, g_tb});
146 end
147 endmodule

```

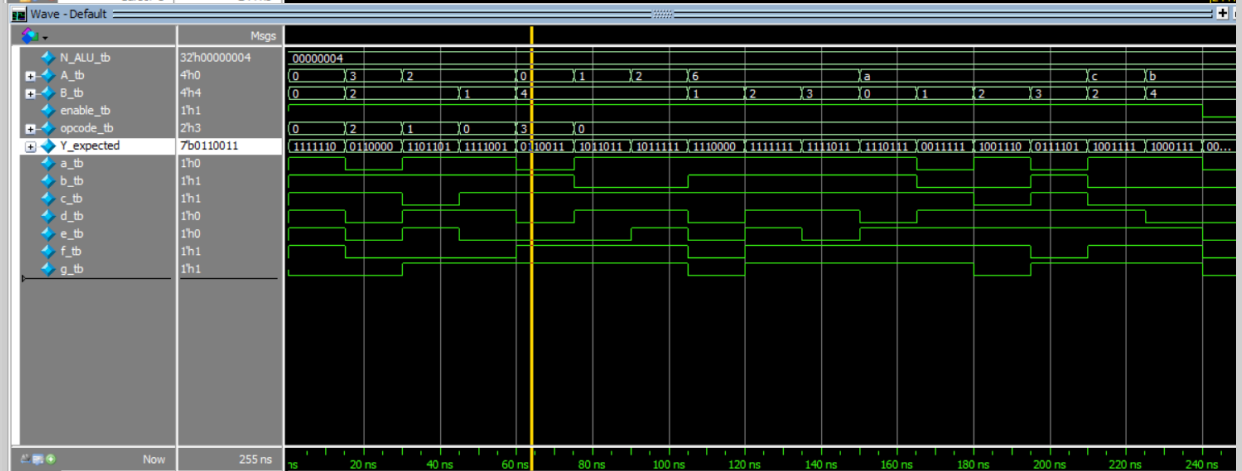 

```

|VSIM 11> run -all
# A_tb=0000, B_tb=0000, opcode_tb=00, enable_tb=1, Y_expected=1111110, {a_tb, b_tb, c_tb, d_tb, e_tb, f_tb, g_tb}=1111110
# A_tb=0011, B_tb=0010, opcode_tb=10, enable_tb=1, Y_expected=0110000, {a_tb, b_tb, c_tb, d_tb, e_tb, f_tb, g_tb}=0110000
# A_tb=0010, B_tb=0010, opcode_tb=01, enable_tb=1, Y_expected=1101101, {a_tb, b_tb, c_tb, d_tb, e_tb, f_tb, g_tb}=1101101
# A_tb=0010, B_tb=0001, opcode_tb=00, enable_tb=1, Y_expected=1111001, {a_tb, b_tb, c_tb, d_tb, e_tb, f_tb, g_tb}=1111001
# A_tb=0000, B_tb=0100, opcode_tb=11, enable_tb=1, Y_expected=0110011, {a_tb, b_tb, c_tb, d_tb, e_tb, f_tb, g_tb}=0110011
# A_tb=0001, B_tb=0100, opcode_tb=00, enable_tb=1, Y_expected=1011011, {a_tb, b_tb, c_tb, d_tb, e_tb, f_tb, g_tb}=1011011
# A_tb=0010, B_tb=0100, opcode_tb=00, enable_tb=1, Y_expected=1011111, {a_tb, b_tb, c_tb, d_tb, e_tb, f_tb, g_tb}=1011111
# A_tb=0110, B_tb=0001, opcode_tb=00, enable_tb=1, Y_expected=1110000, {a_tb, b_tb, c_tb, d_tb, e_tb, f_tb, g_tb}=1110000
# A_tb=0110, B_tb=0010, opcode_tb=00, enable_tb=1, Y_expected=1111111, {a_tb, b_tb, c_tb, d_tb, e_tb, f_tb, g_tb}=1111111
# A_tb=0110, B_tb=0011, opcode_tb=00, enable_tb=1, Y_expected=1111011, {a_tb, b_tb, c_tb, d_tb, e_tb, f_tb, g_tb}=1111011
# A_tb=1010, B_tb=0000, opcode_tb=00, enable_tb=1, Y_expected=1110111, {a_tb, b_tb, c_tb, d_tb, e_tb, f_tb, g_tb}=1110111
# A_tb=1010, B_tb=0001, opcode_tb=00, enable_tb=1, Y_expected=0011111, {a_tb, b_tb, c_tb, d_tb, e_tb, f_tb, g_tb}=0011111
# A_tb=1010, B_tb=0010, opcode_tb=00, enable_tb=1, Y_expected=1001110, {a_tb, b_tb, c_tb, d_tb, e_tb, f_tb, g_tb}=1001110
# A_tb=1010, B_tb=0011, opcode_tb=00, enable_tb=1, Y_expected=0111101, {a_tb, b_tb, c_tb, d_tb, e_tb, f_tb, g_tb}=0111101
# A_tb=1100, B_tb=0010, opcode_tb=00, enable_tb=1, Y_expected=1001111, {a_tb, b_tb, c_tb, d_tb, e_tb, f_tb, g_tb}=1001111
# A_tb=1011, B_tb=0100, opcode_tb=00, enable_tb=1, Y_expected=1000111, {a_tb, b_tb, c_tb, d_tb, e_tb, f_tb, g_tb}=1000111
# A_tb=1011, B_tb=0100, opcode_tb=00, enable_tb=0, Y_expected=0000000, {a_tb, b_tb, c_tb, d_tb, e_tb, f_tb, g_tb}=0000000
# ** Note: $stop      : C:/questasim64_2021.1/examples/SEVEN_SEGNET_tb.v(141)
#      Time: 255 ns  Iteration: 0  Instance: /SEVEN_SEGMENT_tb
# Break in Module SEVEN_SEGMENT_tb at C:/questasim64_2021.1/examples/SEVEN_SEGNET_tb.v line 141

```

