

Combinational Circuit Design

Design the following circuits using Verilog **and create a testbench (directed or randomized)** for each design to check its functionality.

1)

Design a Verilog module using **generate conditional construct** that takes a 3-bit binary input (A[2:0]) and produces a corresponding encoded output (B[6:0]). The encoding method can be selected using a parameter called USE_GRAY, which can be set to either 1 or 0. If USE_GRAY is set to 1, the module should perform Gray encoding on the input using always block. If USE_GRAY is set to 0, the module should perform one-hot encoding on the input using always block. Default value for USE_GRAY = 1.

One-hot encoding is a way of representing data in a binary string in which only a single bit can be 1, while all others are 0.


Gray encoding, also known as Gray code, is a binary numeral system where consecutive values differ by only one bit. In Gray encoding, each binary number is represented such that only one bit changes from one value to the next, reducing the possibility of errors during transitions.

Decimal	Binary	Gray code	One-hot
0	000	000	0000000
1	001	001	0000001
2	010	011	0000010
3	011	010	0000100
4	100	110	0001000
5	101	111	0010000
6	110	101	0100000
7	111	100	1000000

Write **two testbenches** to verify the functionality of the design in both parameter values. The first testbench should instantiate the design and override the parameter USE_GRAY to be equal 1 and the second testbench to override the USE_GRAY to be equal 0. Both testbenches should be exhaustive testbenches and check the results from the waveforms.

2) Design a 1-to-4 demultiplexer (Demux) using Verilog. The demultiplexer should have a single input (D) and two select inputs (S[1:0]). The output should consist of four signals (Y[3:0]), where the input signal (D) is routed to one of the four outputs based on the select inputs. Write the Verilog code for this demultiplexer and simulate its functionality using an exhaustive self-checking testbench.

Data Input	Select Inputs		Outputs			
D	S ₁	S ₀	Y ₃	Y ₂	Y ₁	Y ₀
D	0	0	0	0	0	D
D	0	1	0	0	D	0
D	1	0	0	D	0	0
D	1	1	D	0	0	0

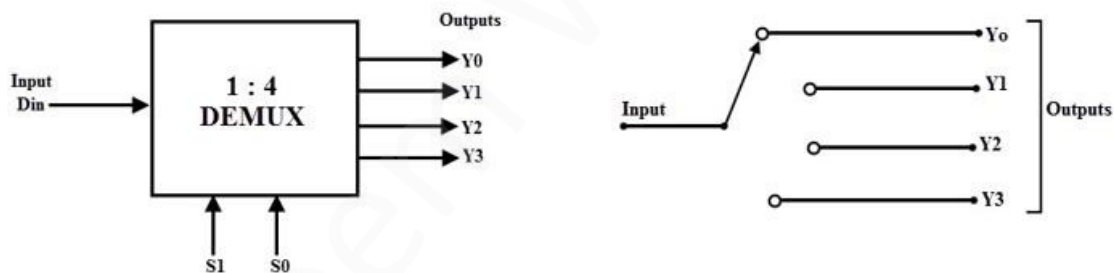

Deliverables: The assignment should be submitted as a PDF file with this format <your_name>_Assignment2

Note that your document should be organized as 2 sections corresponding to each design above, and in each section, I am expecting the Verilog code for the design, testbench and the waveforms snippets